 


Blocking Vs Non Blocking


Code

```
1 module check( input  clk,c,output reg a,b,d  );
2
3
4
5
6
7 always@(posedge clk)
8 begin
9
10
11   a=c;
12
13
14
15 end
16 endmodule
```

Circuit




Simulation

 


Code

```
| module check( input  clk,c,output reg a,b,d  );  
  
| always@(posedge clk)  
| begin  
  
| a<=c;  
  
| end  
| endmodule
```

Circuit

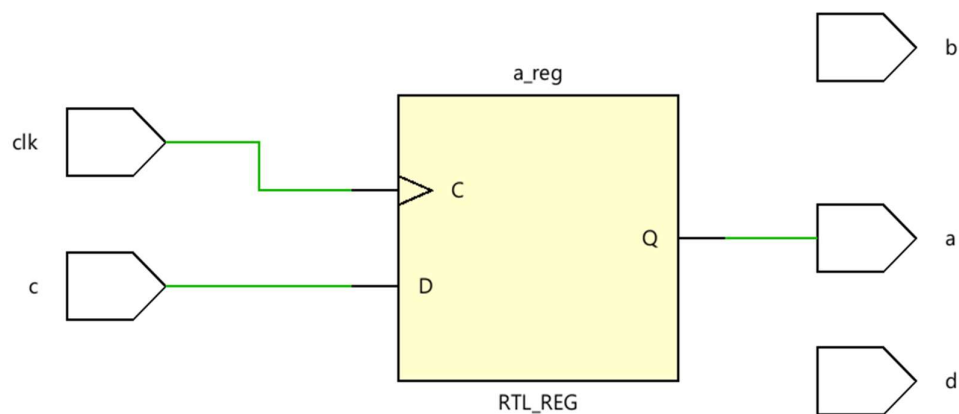

Simulation

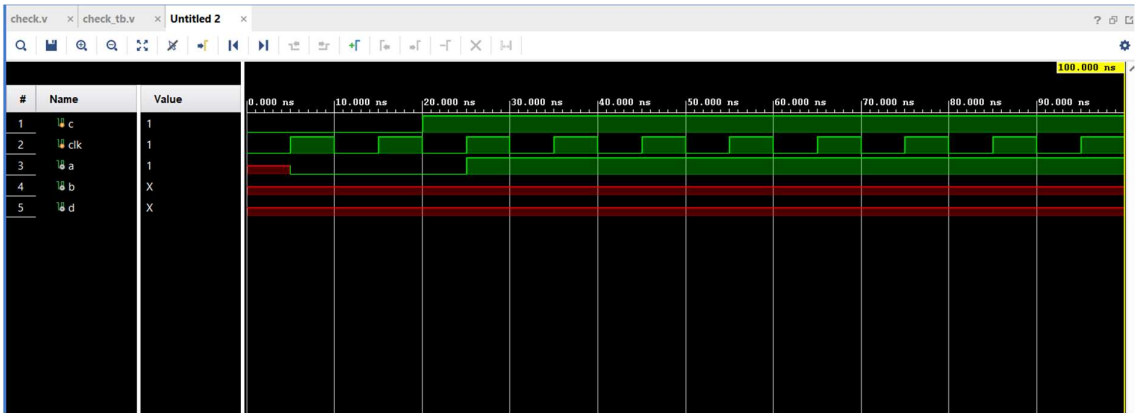

Code


```
module check( input  clk,c,output reg a,b,d  );

always@(posedge clk)
begin


a=c;
b=a;
d=b;

end
endmodule
```

Circuit

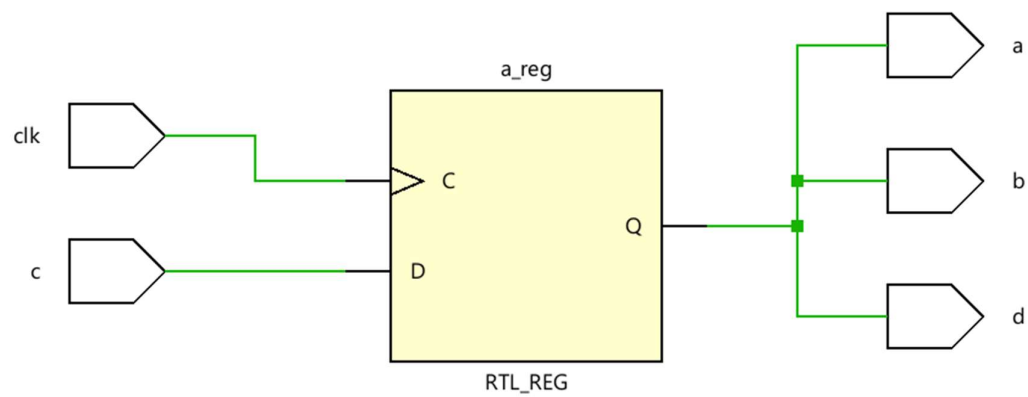

Simulation

 

Code


```
) module check( input  clk,c,output reg a,b,d  );

) always@(posedge clk)
) begin


    a<=c;
    b<=a;
    d<=b;

) end
) endmodule
```

Circuit

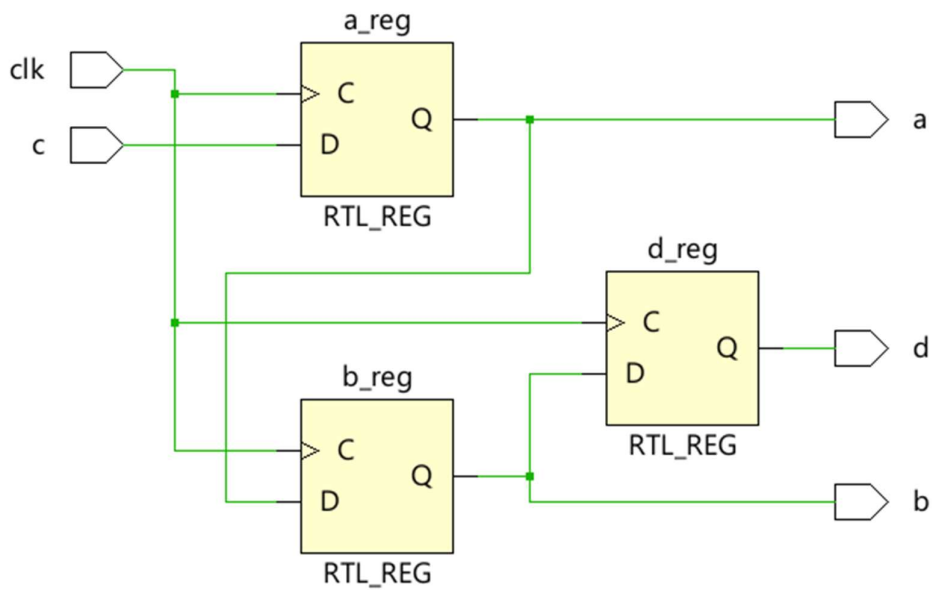

Simulation

 


Code

```
module check( input  clk,c,output reg a,b,d  );


always@(posedge clk)
begin
a=c;
if(a==0)
b<=1;
else if(a==1)
b<=0;
//d=b;

end
endmodule
```

Circuit

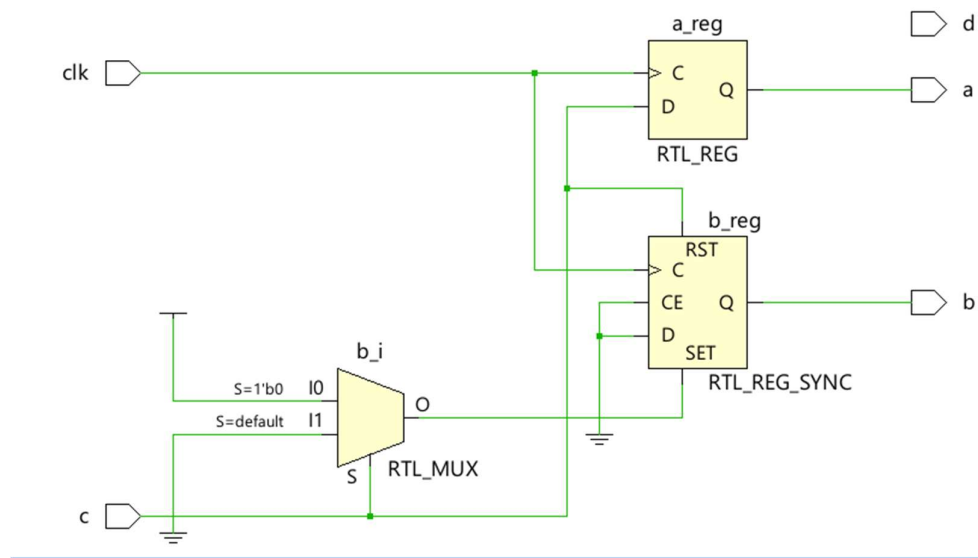


Simulation

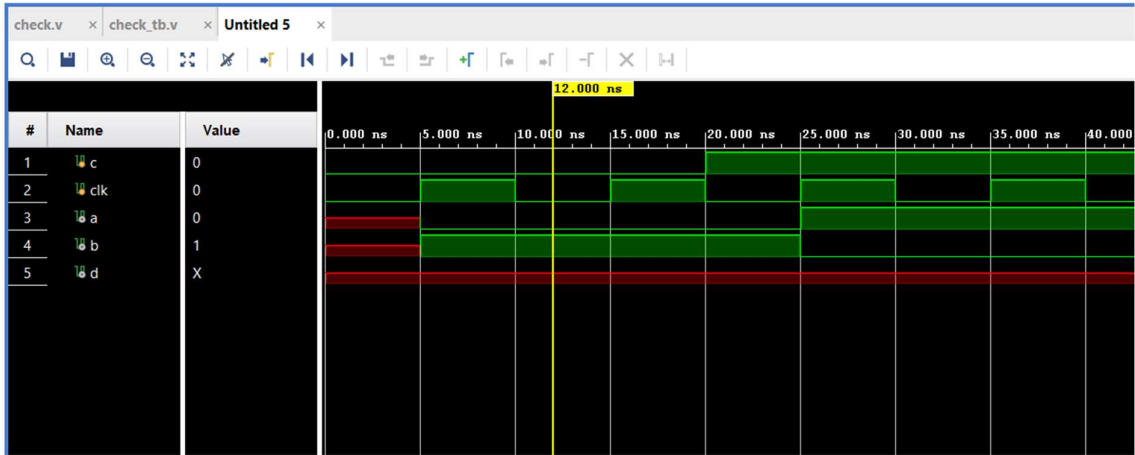


Code

```
module check( input  clk,c,output reg a,b,d  );
|
|
|
|
| always@(posedge clk)
| begin
| a=c;
| if (a==0)
| b=1;
| else if (a==1)
| b=0;
| //d=b;
|
|
| end
| endmodule
```

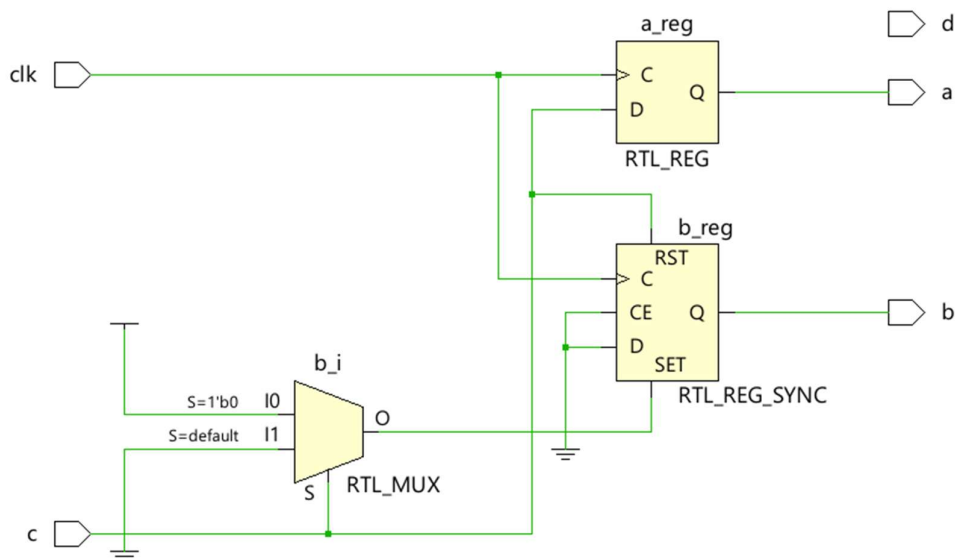Circuit (no change if compared to previous one)



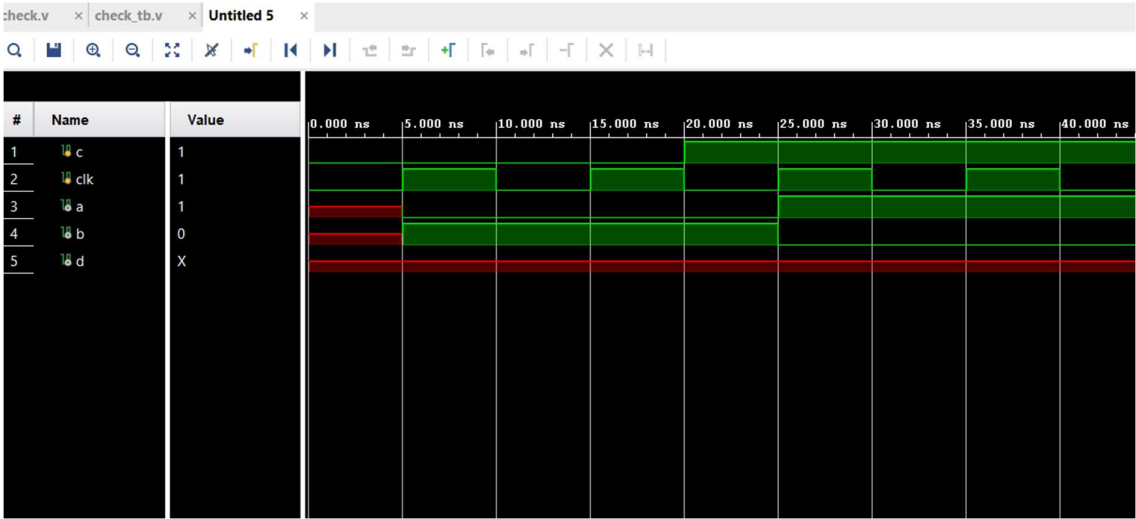Simulation(no change if compared to previous one)




Code

```
module check( input  clk,c,output reg a,b,d  );


always@(posedge clk)
begin
a<=c;
if(a==0)
b<=1;
else if(a==1)
b<=0;
//d=b;

end
endmodule
```

Circuit

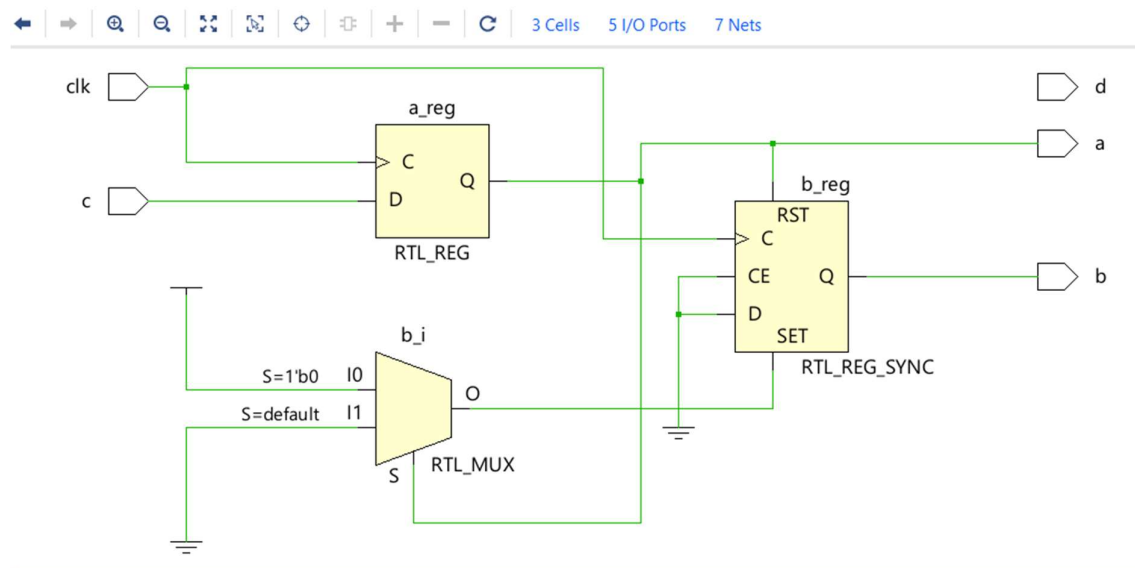


Simulation

 


Code

```
module check( input  clk,c,output reg a,b,d  );  
  
    always@(posedge clk)  
    begin  
        a<=c;  
        if (a==0)  
            b=1;  
        else if (a==1)  
            b=0;  
        //d=b;  
  
    end  
endmodule
```

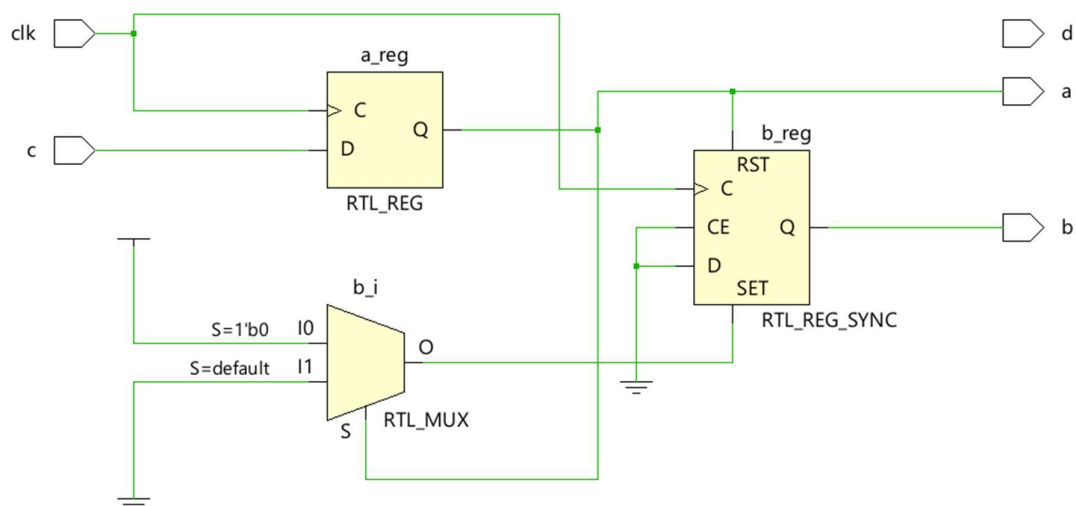Circuit (no change if compared to previous one)



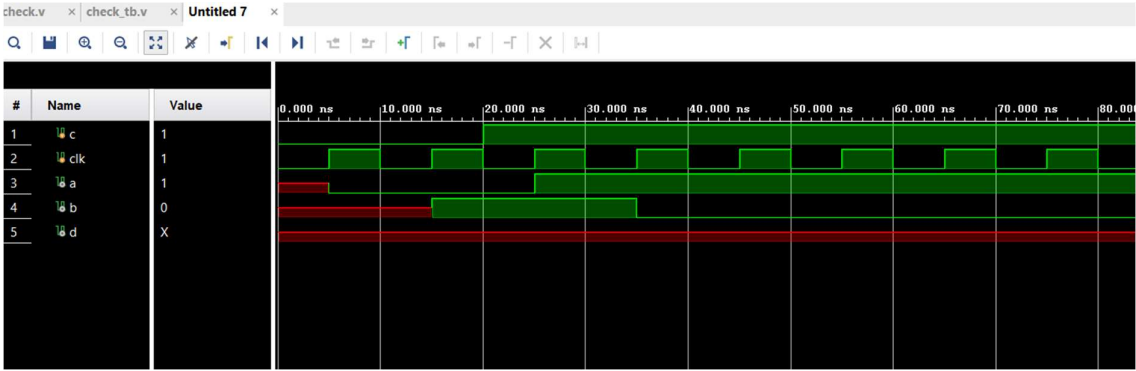
Simulation (no change if compared to previous one)




Code

```
12
13 module check( input  clk,c,output reg a,b,d  );
14
15
16
17 always@(posedge clk)
18 begin
19   a<=c;
20   if(a==0)
21     b<=1;
22   else if(a==1)
23     b<=0;
24   //d=b;
25
26
27 end
28 endmodule
29
```

Circuit

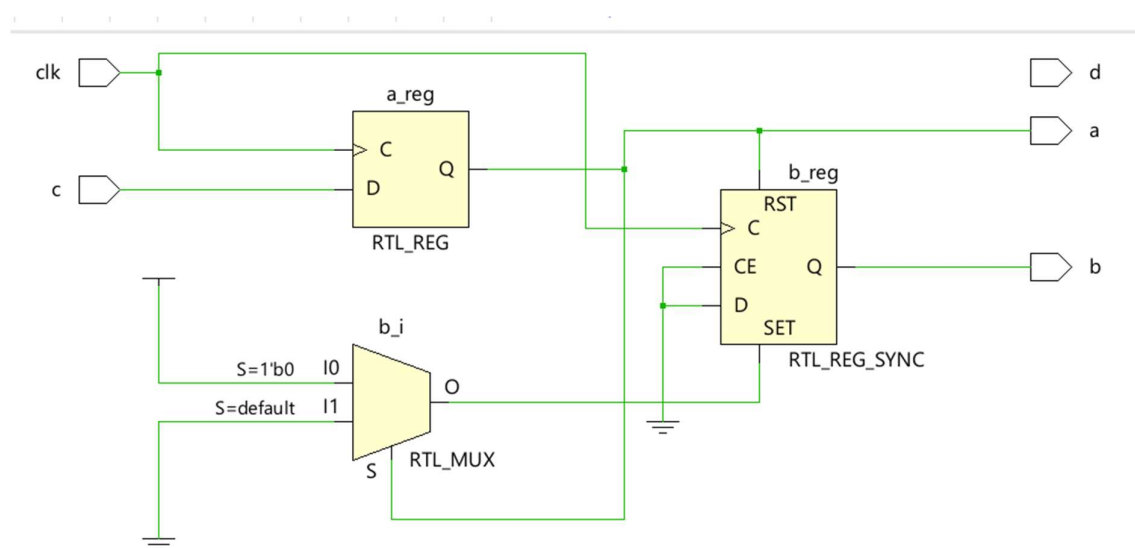

Simulation

 


Code

```
module check( input  clk,c,output reg a,b,d  );


always@(posedge clk)
begin
a<=c;
if(a==0)
b<=1;
else if(a==1)
b<=0;
d<=b;

end
endmodule
```

Circuit

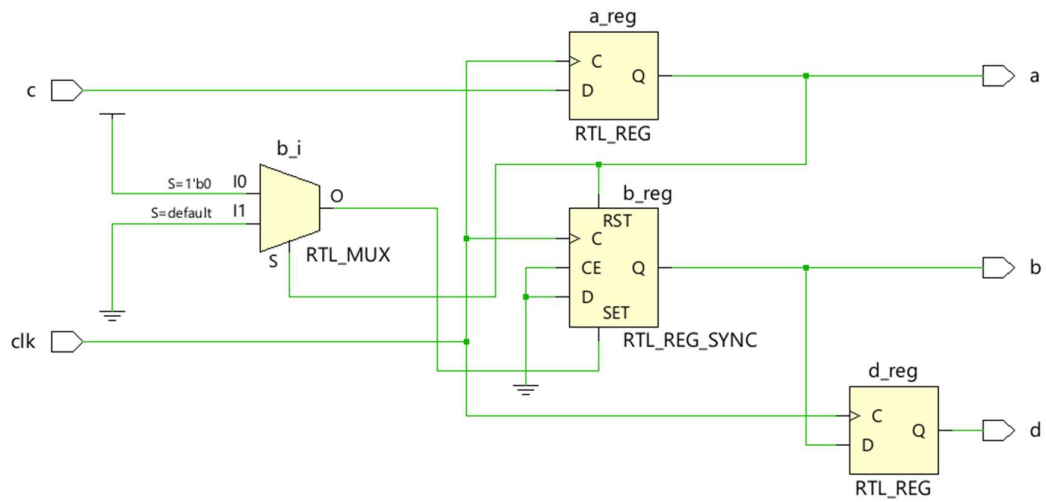

Simulation

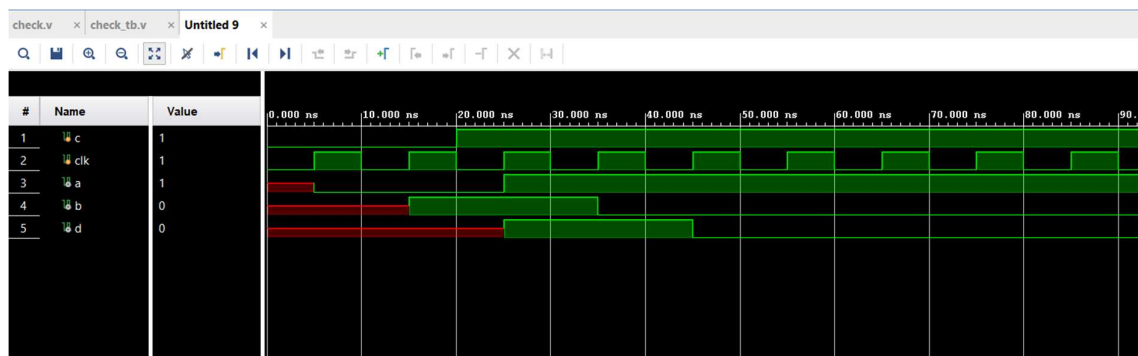


Code

```
module check( input  clk,c,output reg a,b,d  );

always@(posedge clk)
begin
a<=c;
if (a==0)
b<=1;
else if(a==1)
b<=0;
d=b;

end
endmodule
```

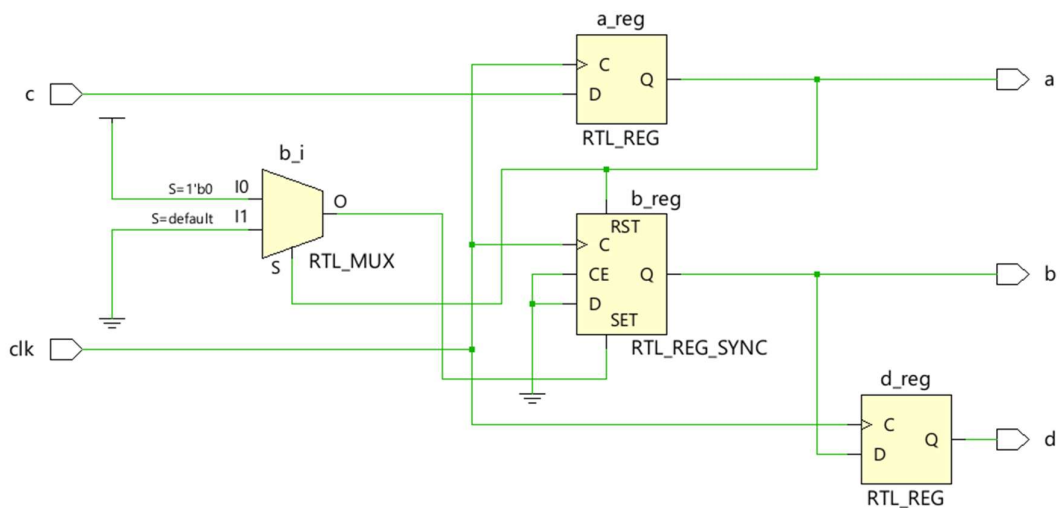Circuit (no change if compared to previous one)




Simulation (no change if compared to previous one)




Code

```
2 |  
3 | module check( input  clk,c,output reg a,b,d  );  
4 |  
5 |  
6 |  
7 | always@(posedge clk)  
8 | begin  
9 |   a<=c;  
10 |   if(a==0)  
11 |     b=1;  
12 |   else if(a==1)  
13 |     b=0;  
14 |     d=b;  
15 |  
16 |  
17 | end  
18 | endmodule  
19 |
```

Circuit

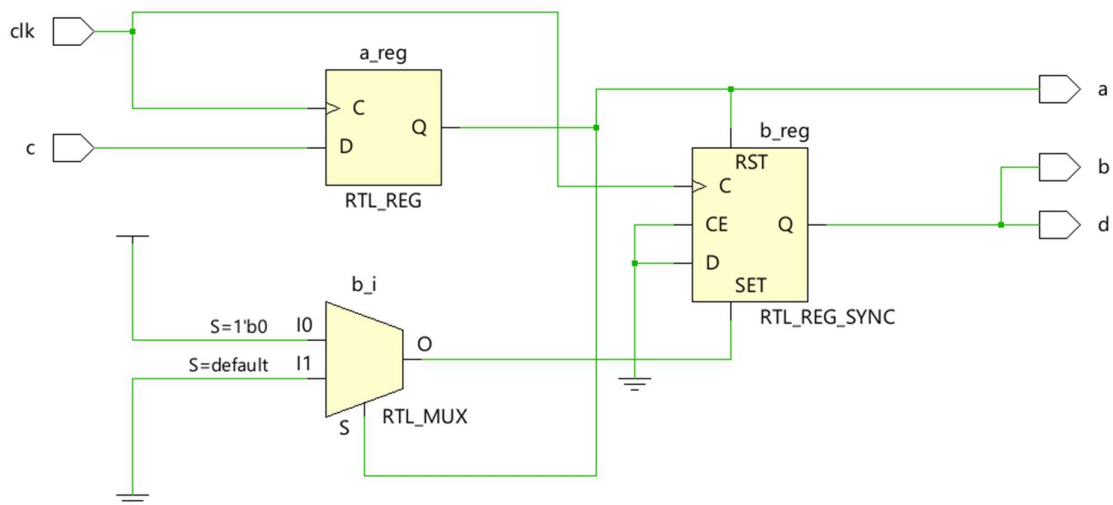


Simulation

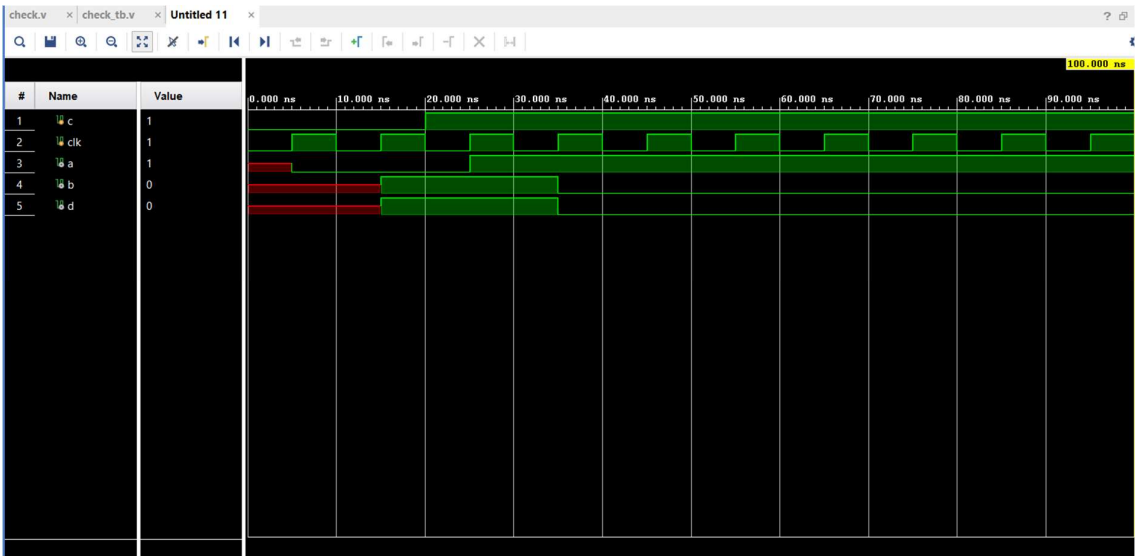


Code

```
module check( input  clk,c,output reg a,b,d  );  
  
    always@(posedge clk)  
    begin  
        a<=c;  
        if(a==0)  
            b=1;  
        else if(a==1)  
            b=0;  
        d<=b;  
    end  
end  
endmodule
```

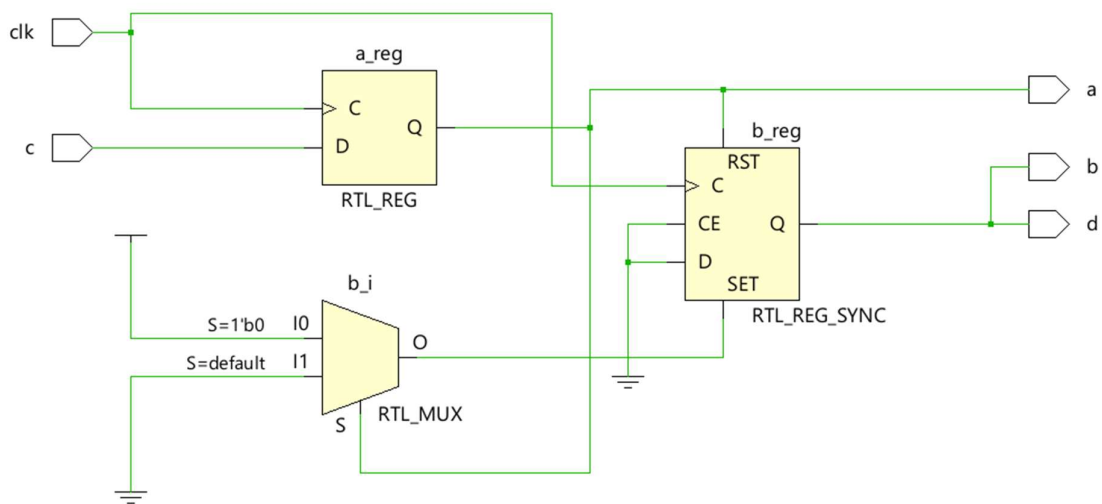Circuit (no change if compared to previous one)



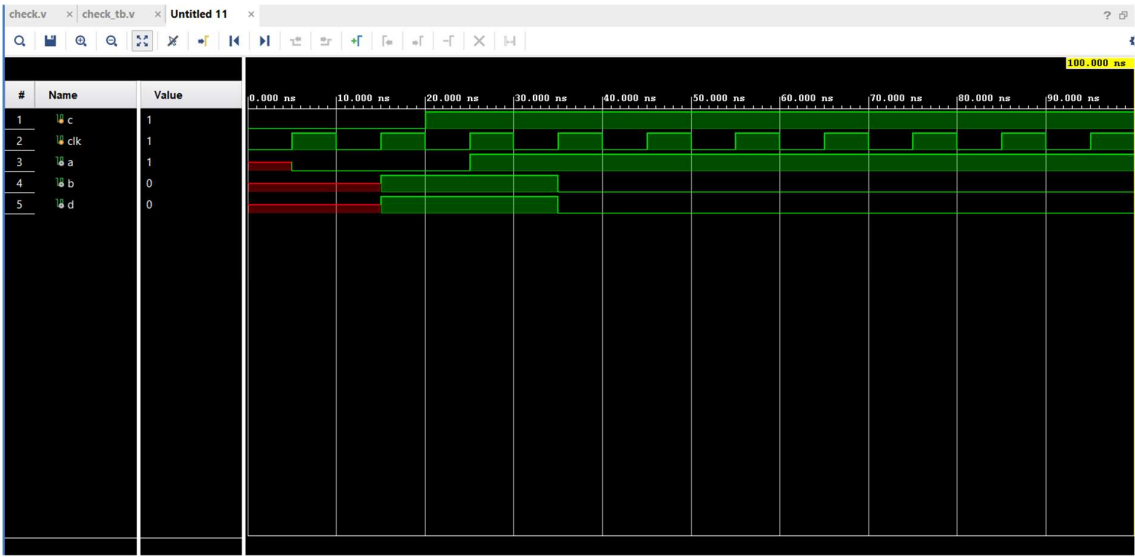
Simulation (no change if compared to previous one)




Code

```
module check( input  clk,c,output reg a,b,d  );  
  
always@(posedge clk)  
begin  
a=c;  
if(a==0)  
b=1;  
else if(a==1)  
b=0;  
d<=b;  
  
end  
endmodule
```

Circuit

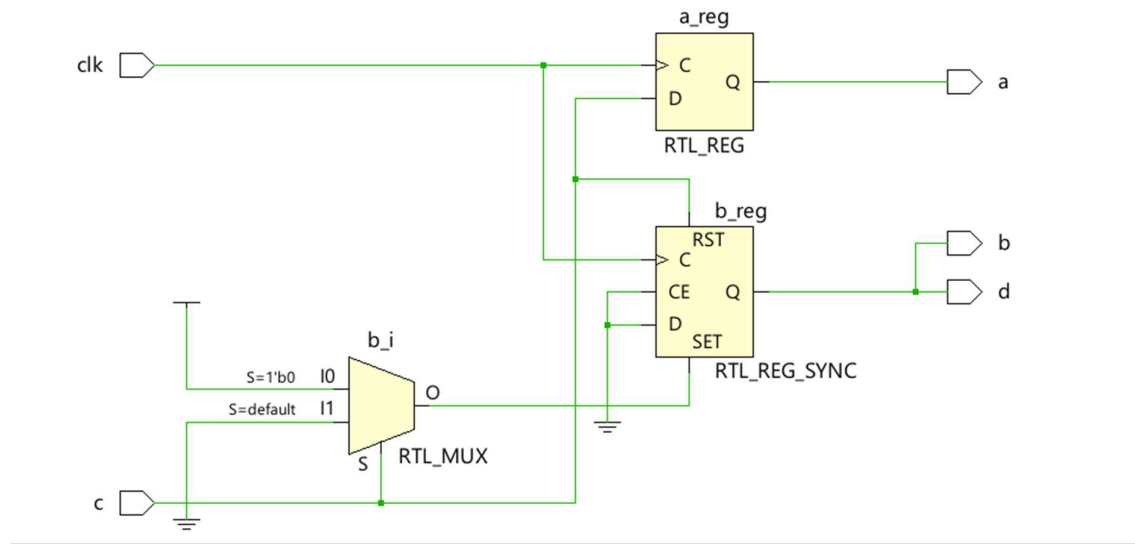

Simulation

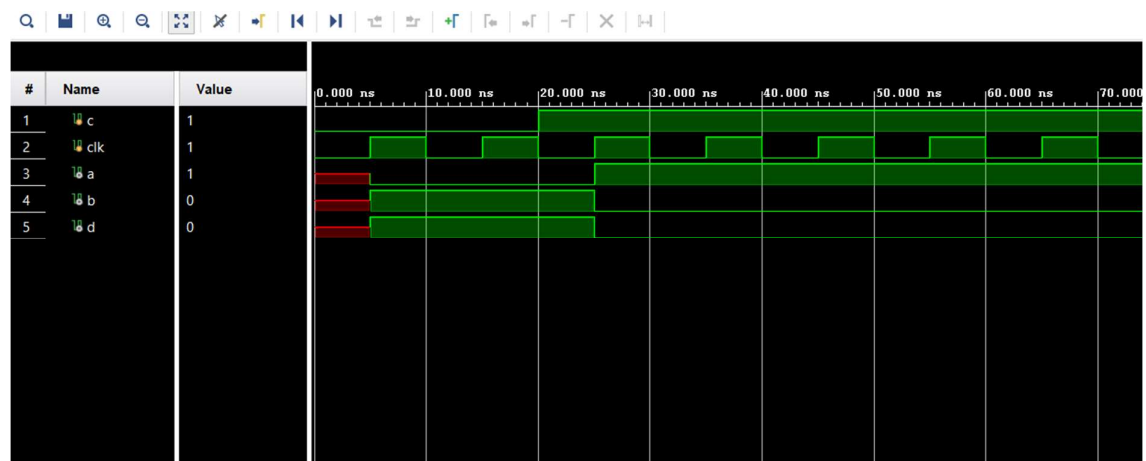


Code

```
) module check( input  clk,c,output reg a,b,d  );


) always@(posedge clk)
) begin
    a=c;
) if(a==0)
    b<=1;
) else if(a==1)
) b<=0;
    d<=b;

) end
) endmodule
```

Circuit

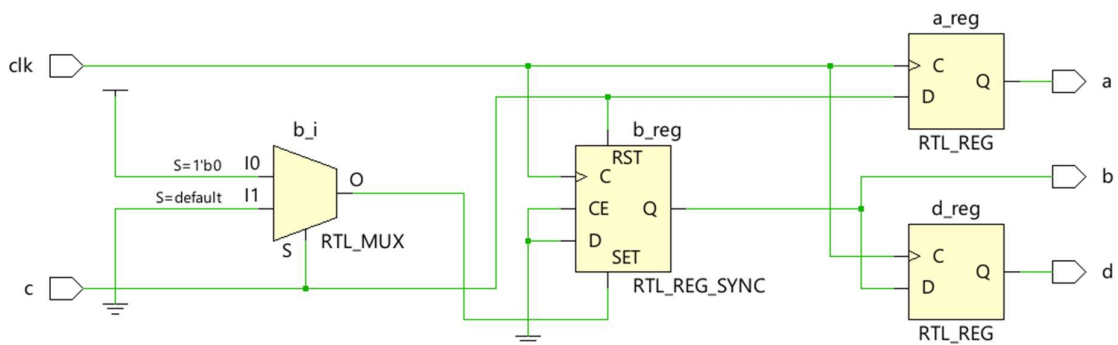

Simulation

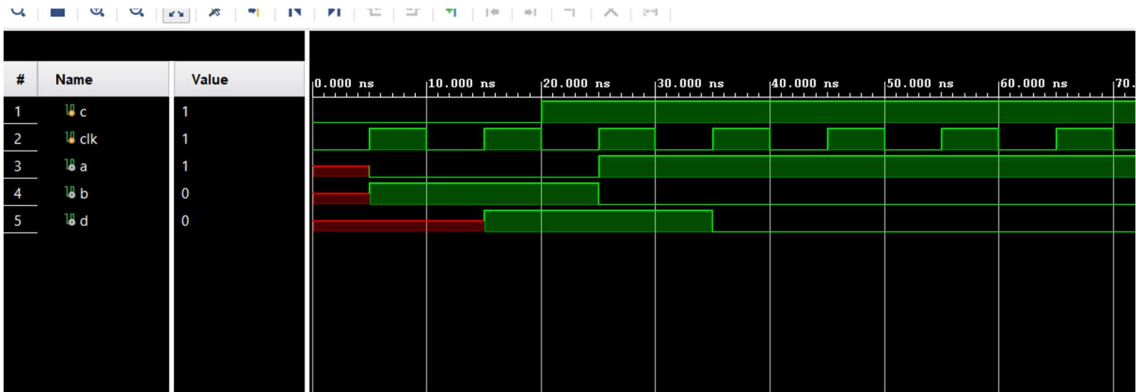

Code

```
module check( input  clk,c,output reg a,b,d  );
```

```
    always@(posedge clk)
```

```
    begin
```

```
        a=c;
```

```
        if(a==0)
```

```
            b<=1;
```

```
        else if(a==1)
```


```
            b<=0;
```

```
            d=b;
```

```
    end
```

```
endmodule
```

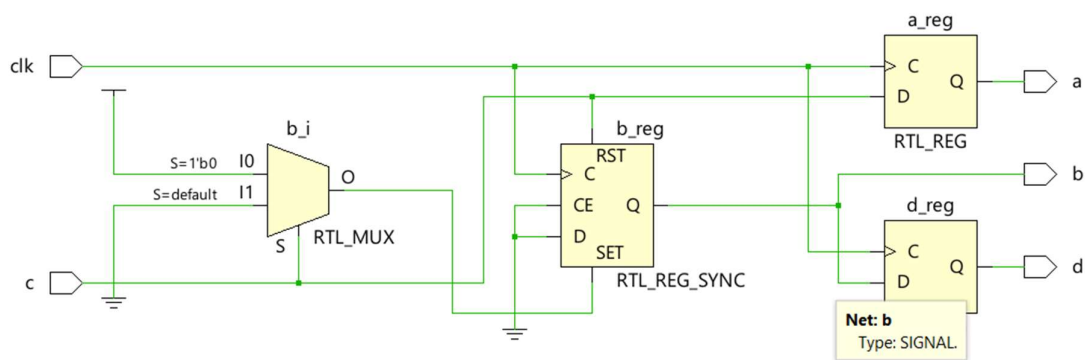Circuit (no change if compared to previous one)



Simulation (no change if compared to previous one)

